

# Project Documentation

## IEC-Bus Breakout Board

Project number: 206

Revision: 0

Date: 31.03.2023

# IEC-Bus Breakout Board Rev. 0

## Module Description

This board serves as a breakout board for the Commodore IEC-bus. It already contains the required driver IC (74LS06) and a 74LS04 as a receiver (which resembles the original Commodore hardware).

The purpose is connecting the IEC-bus to microcontroller (modules) like an Arduino, as Raspberry Pi or a Raspberry Pi pico microcontroller. It would be possible to wire up a Pi1541 drive emulator.

For the Raspberry Pis, a level shifter5 circuit is required, which is also implemented in this board. It can either be placed on-board as SMD components (8x 10k 0805 resistors and 4x BSS138 SOT-23 transistors). Alternatively, a pretty common level shifter module can be soldered to the board or put on soldered in socket strips.

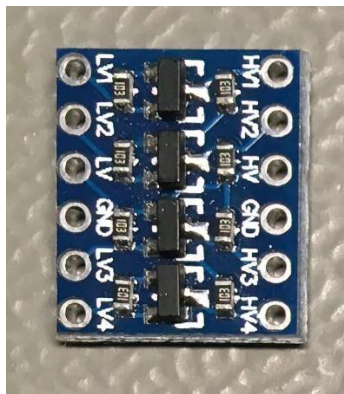


Figure 1: Level shifter module board

The dimensions of the level shifter module are approximately 12.7mm x 15.3mm. It is almost a standard module, which is available from AliExpress, Ebay, Amazon etc.

## Pinouts

### J1 - IEC-Bus

Lumberg 010599 06, 6p DIN receptacles

Pin	Signal
1	/SRQ (not used in this design)
2	GND
3	ATN
4	CLK
5	DATA
6	/RESET

### J4 - +5VDC Power

5,5mm/2,5mm barrel connector

Pin	Signal
Inner lead	+5VDC
Outer lead	GND

## J2 - 3.3V Level Pin Header

1x9 pin header (2.54mm)

Pin	Signal	Direction
1	GND	-
2	ATN_IN	$\mu$ C input
3	CLK_IN	$\mu$ C input
4	$\overline{\text{CLK\_OUT}}$	$\mu$ C output
5	DATA_IN	$\mu$ C input
6	$\overline{\text{DATA\_OUT}}$	$\mu$ C output
7	$\overline{\text{RESET\_IN}}$	$\mu$ C input
8	+3.3V	-
9	+5V	-

## J3 – 5V (TTL) Level Pin Header

1x9 pin header (2.54mm)

Pin	Signal	Direction
1	GND	-
2	ATN_IN (5V)	$\mu$ C input
3	CLK_IN (5V)	$\mu$ C input
4	$\overline{\text{CLK\_OUT}}$	$\mu$ C output
5	DATA_IN (5V)	$\mu$ C input
6	$\overline{\text{DATA\_OUT}}$	$\mu$ C output
7	$\overline{\text{RESET\_IN}}$ (5V)	$\mu$ C input
8	Not connected	-
9	+5V	-

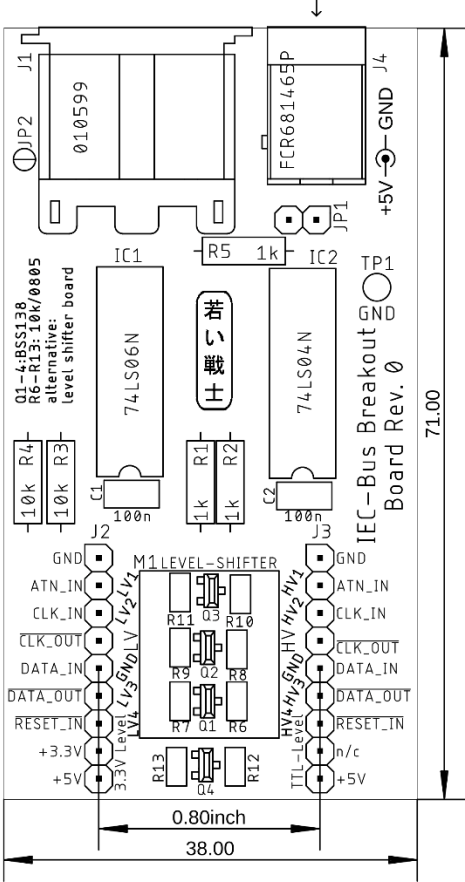


Figure 2: Dimensions of the IEC-bus breakout board

The distance of the pin headers J2 and J3 is 800mil. The pin headers can be place on the component side or the solder side of the board to fit it on a bread board. The width might be too wide to allow access to the receptacle rows. Standard DuPont wires can also serve to connect the board to the micro controller or a Raspberry Pi.


## Revision History

## Rev. 0


- **Untested** prototype



Sven Petersen 2023	Doc.-No.: 206-2-01-00	
	Cu: 35μ	Cu-Layers: 2
IEC-Breakout		
21.03.2023 20:13		Rev.: 0
placement component side		

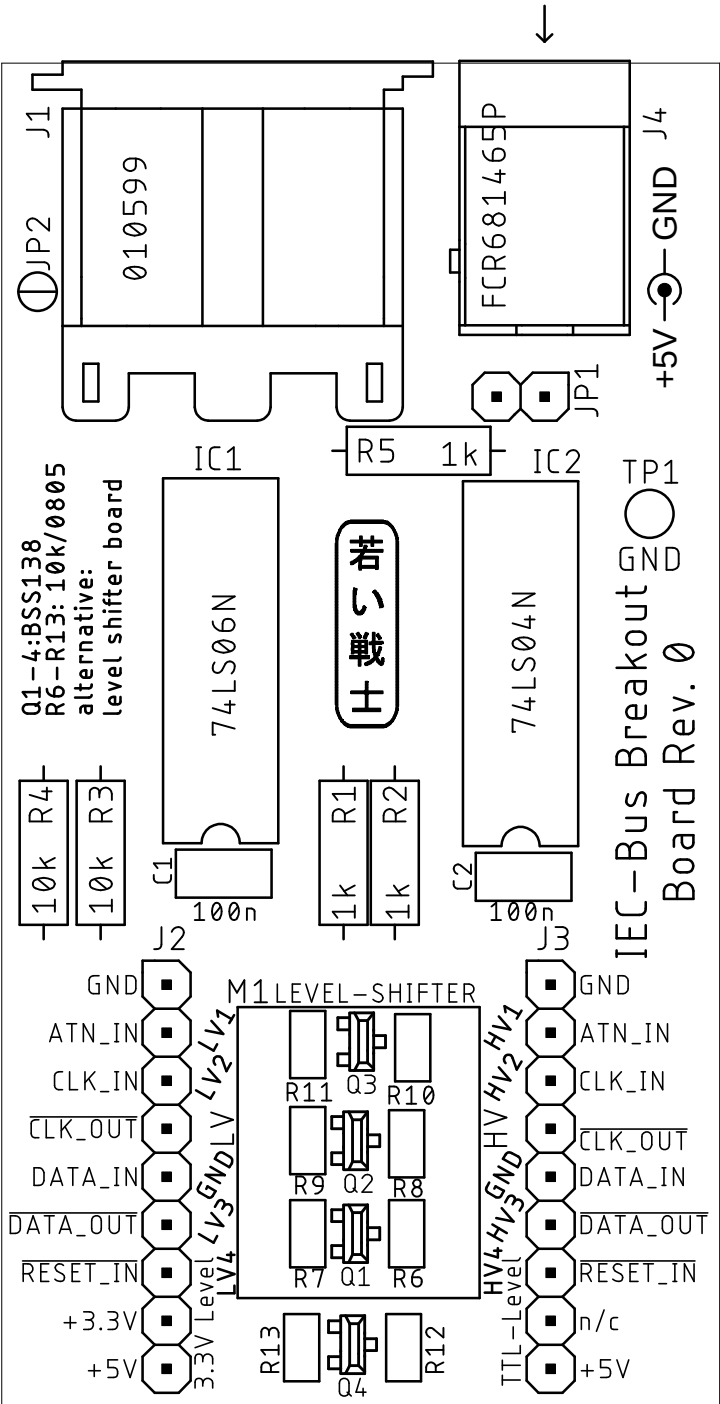

Sven Petersen 2023	Doc.-No.: 206-2-01-00	
	Cu: 35μ	Cu-Layers: 2
IEC-Breakout		
21.03.2023 20:13		Rev.: 0
placement component side		

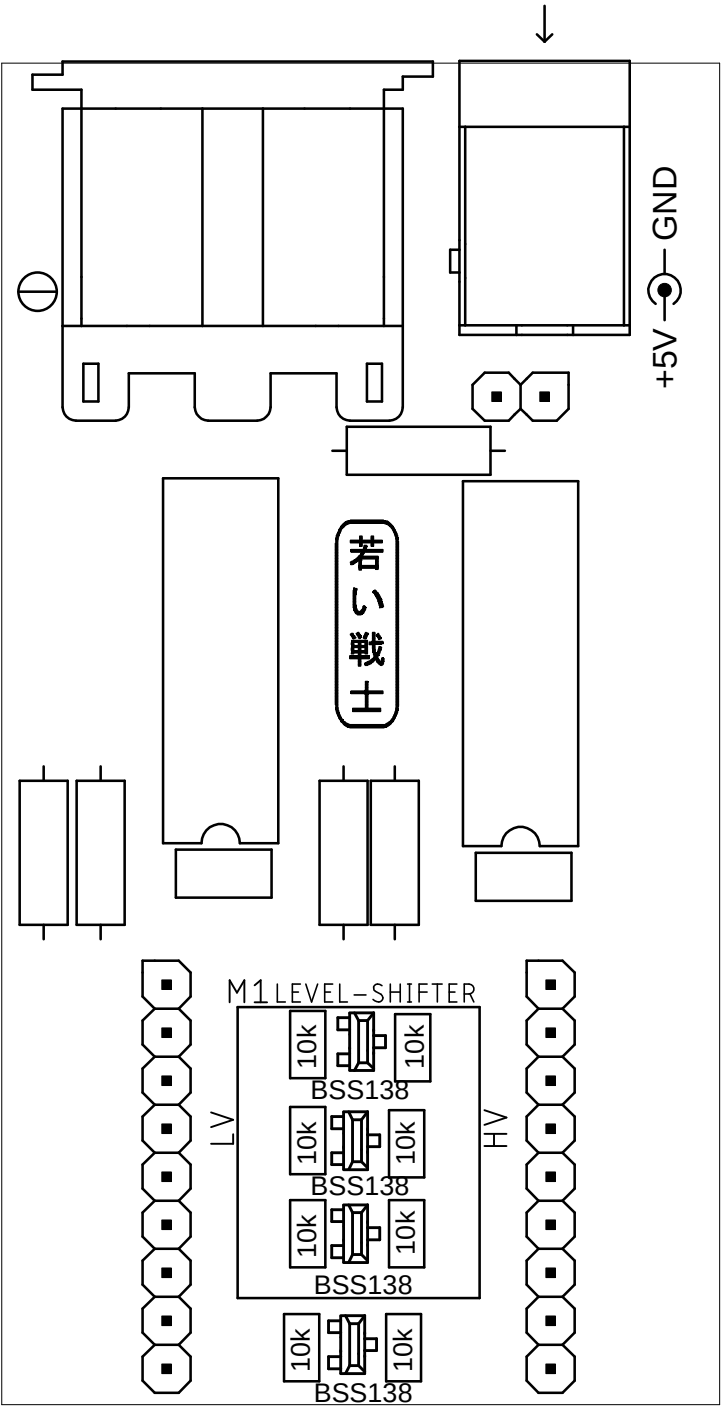


Sven Petersen 2023	Doc.-No.: 206-2-01-00	
	Cu: 35μ	Cu-Layers: 2
IEC-Breakout		
21.03.2023 20:13		Rev.: 0
placement order		







Sven Petersen 2023	Doc.-No.: 206-2-01-00	
	Cu: 35μ	Cu-Layers: 2
IEC-Breakout		
21.03.2023 20:13		Rev.: 0
top		

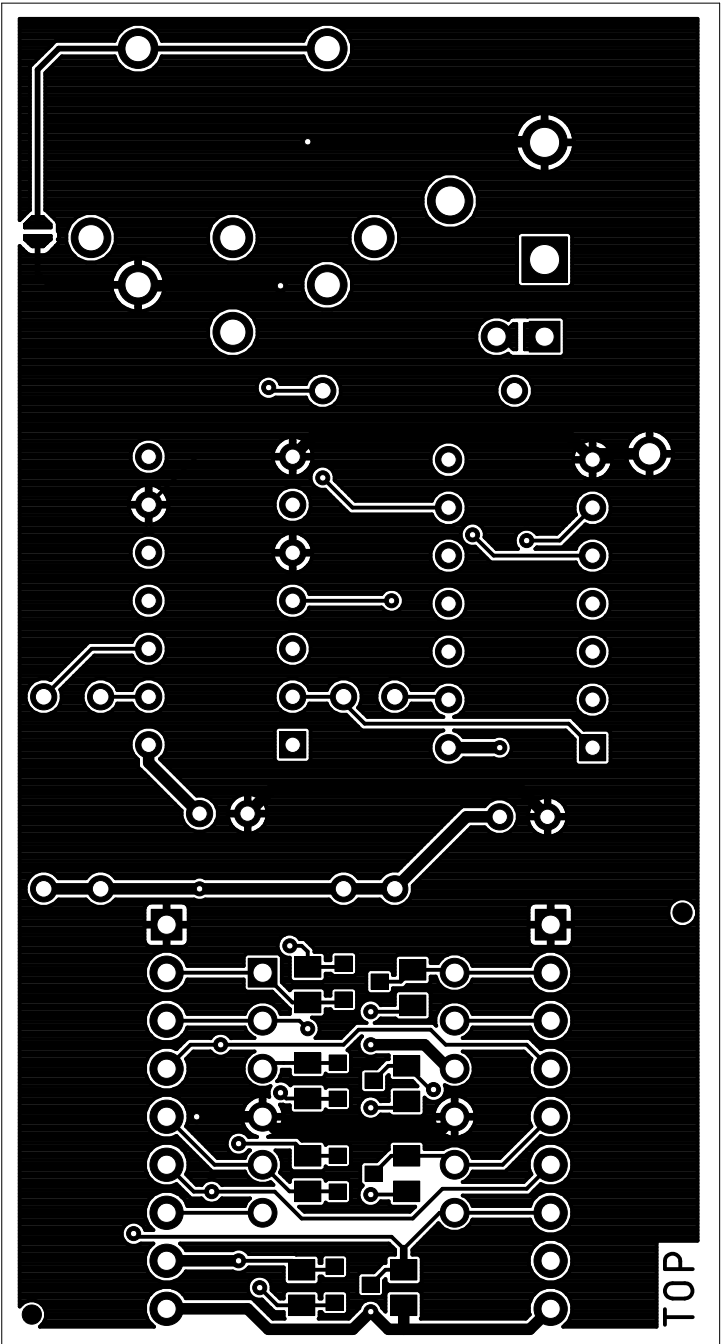


Sven Petersen 2023	Doc.-No.: 206-2-01-00	
	Cu: 35μ	Cu-Layers: 2
IEC-Breakout		
21.03.2023 20:13		Rev.: 0
bottom		

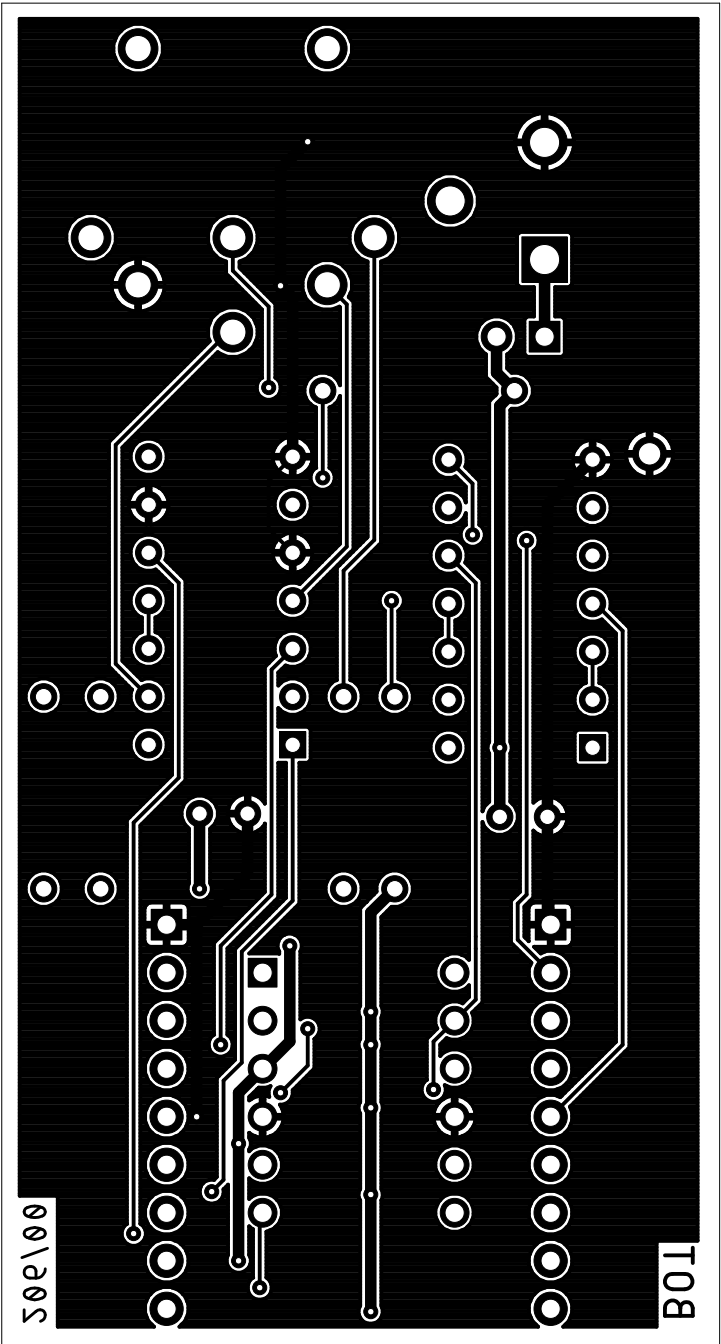


Sven Petersen 2023	Doc.-No.: 206-2-01-00	
	Cu: 35μ	Cu-Layers: 2
IEC-Breakout		
21.03.2023 20:13		Rev.: 0
stopmask component side		

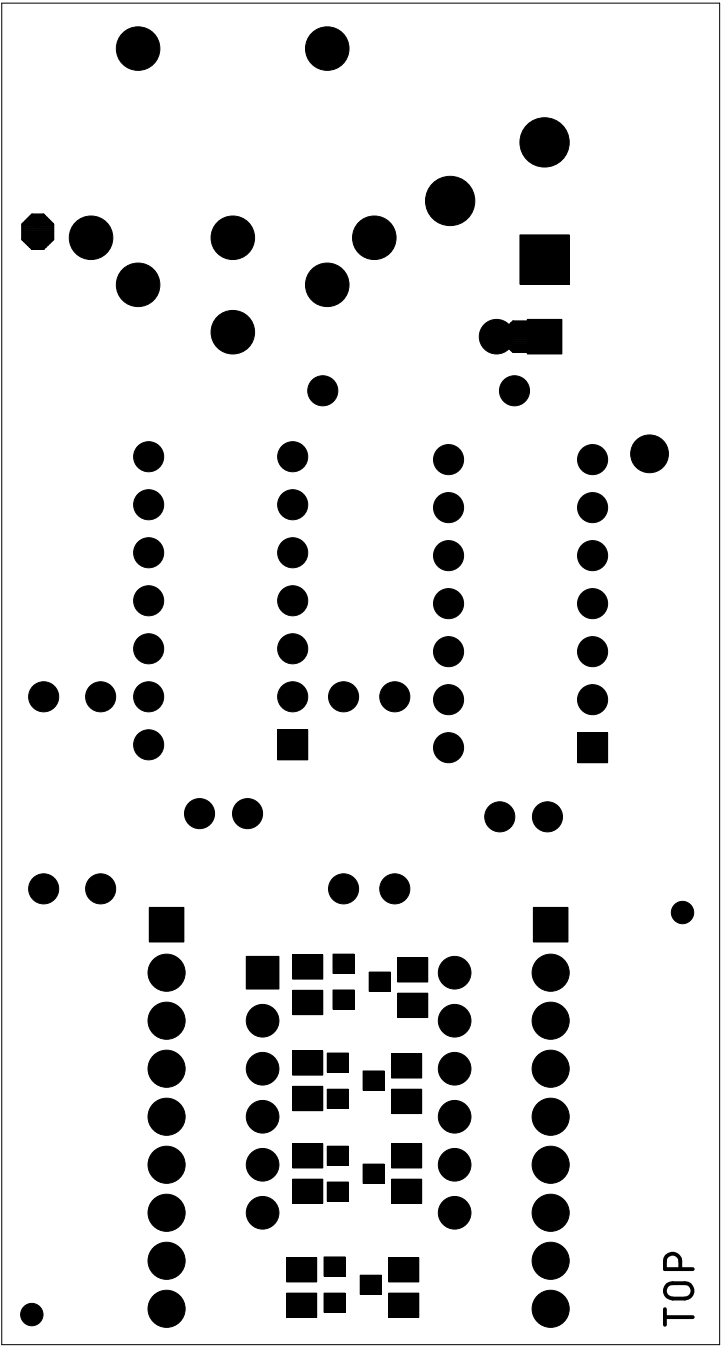

Sven Petersen 2023	Doc.-No.: 206-2-01-00	
	Cu: 35μ	Cu-Layers: 2
IEC-Breakout		
21.03.2023 20:13		Rev.: 0
stopmask solder side		

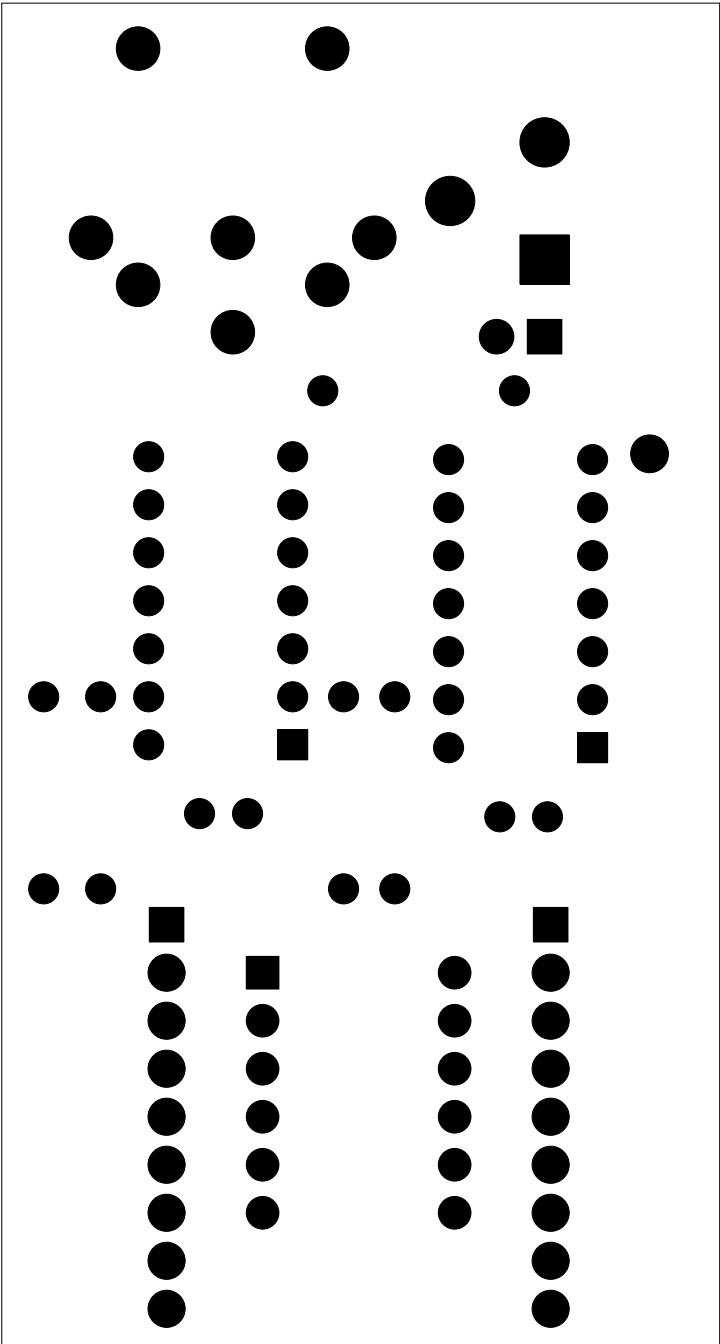

Sven Petersen 2023	Doc.-No.: 206-2-01-00	
	Cu: 35μ	Cu-Layers: 2
IEC-Breakout		
21.03.2023 20:13		Rev.: 0
placement component side		measures

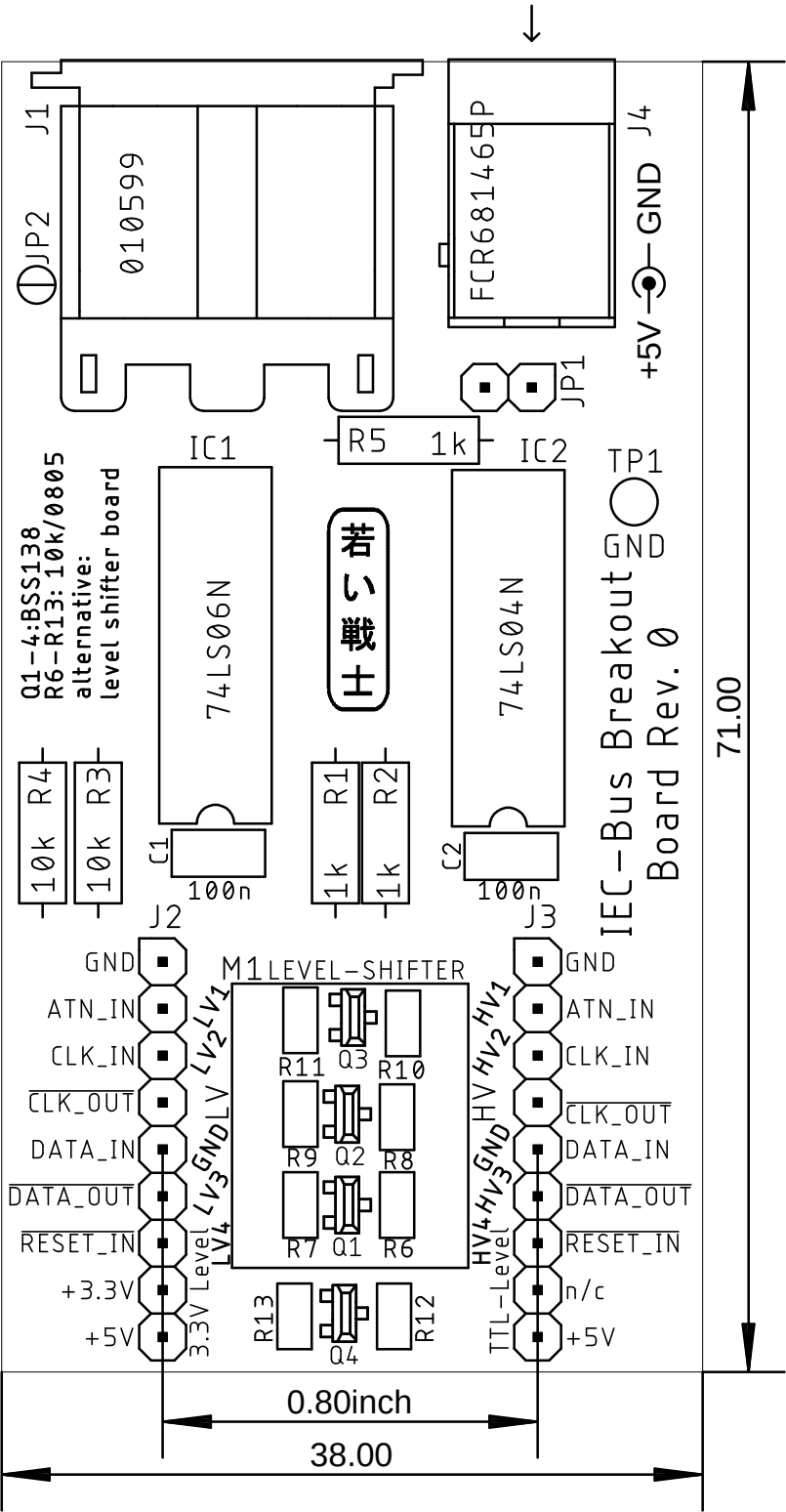

# IEC-Bus Breakout Board Rev. 0

## Bill of Material Rev. 0.0

Pos.	Qty	Value	Footprint	Ref.-No.	Comment
1	1	206-2-01-00	2 Layer	PCB Rev. 0	2 layer, Cu 35μ, HASL, 71.0mm x 38.0mm, 1.6mm FR4
	2	1x9 pin header, 2.54mm	1X09	J2, J3	standard pin header
	1	010599	10599	J1	Lumberg, e.g. Reichelt 010599 06, tme.eu: 0105-06
	2	100n	C-2,5	C1, C2	100n/50V ceramic capacitor, 2.54mm pitch
	8	10k	0805	R6, R7, R8, R9, R10, R11, R12, R13	SMD 0805, 5% or better, for on-board level shifter
	2	10k	R-10	R3, R4	THT resistor, 0.5W, 5%
	3	1k	R-10	R1, R2, R5	THT resistor, 0.5W, 5%
	1	74LS04N	DIL-14	IC2	Logic IC (TTL)
	1	74LS06N	DIL-14	IC1	Logic IC (TTL)
	4	BSS138	SOT23	Q1, Q2, Q3, Q4	MOSFET, for on-board level shifter
	1	COMBI_2P	COMBI-2P	JP1	for power switch, or solderbridge for always on
	1	FCR681465P	FCR681465P	J4	Cliff, Reichelt: CLIFF FCR681465P, tme.eu: FCR681465P
	1	L1,2_R	1,2MM_R	TP1	dnp, GND pin for debugging purposes
	1	LEVEL-SHIFTER	L-SHIFTER	M1	Level shifter module, in case, the onboard level shifter circuit is not placed